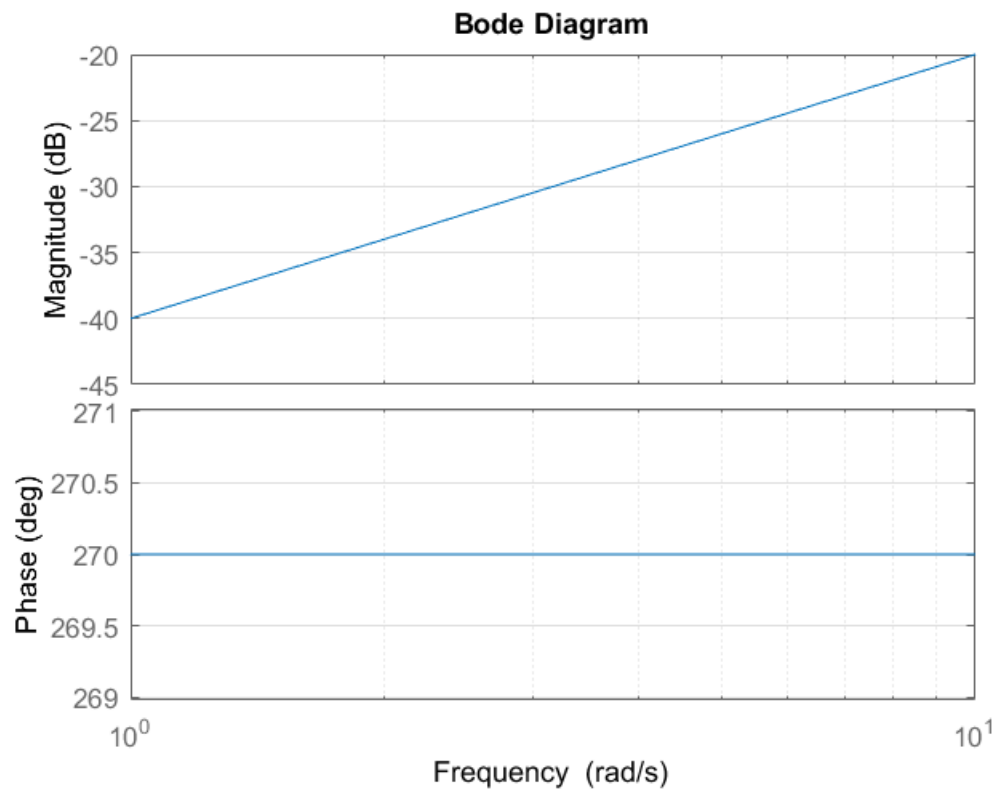

Problem 1b

```
clear all;  
close all;  
clc  
  
R=1e3;  
C=10e-6;  
  
num=[-R*C, 0];  
den=1;  
trans=tf(num,den);  
bode(trans)  
grid minor
```



Published with MATLAB® R2017a